

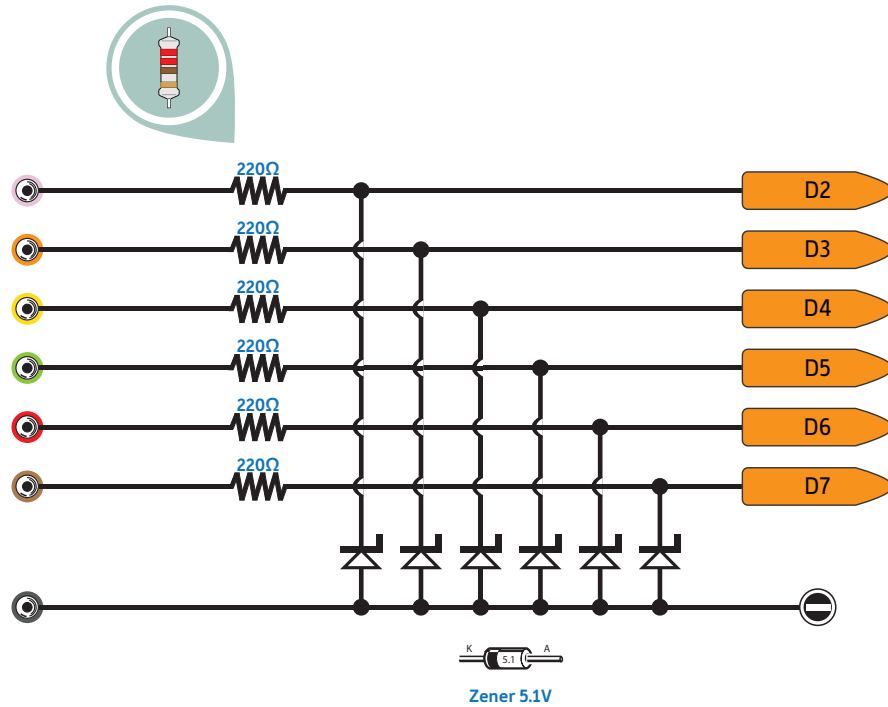


Arduino Logic Analyzer

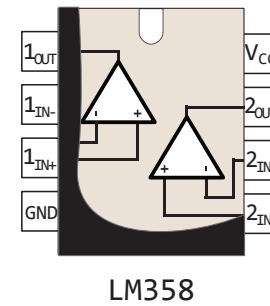


i
See instructions
at
la.pighixxx.com

Current Sense

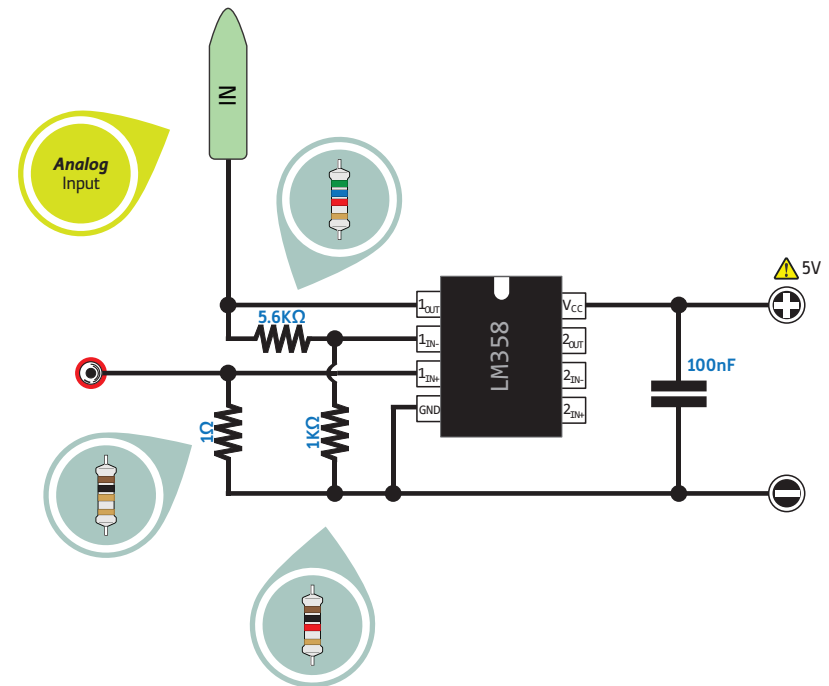

Arduino Component Tester (basic)

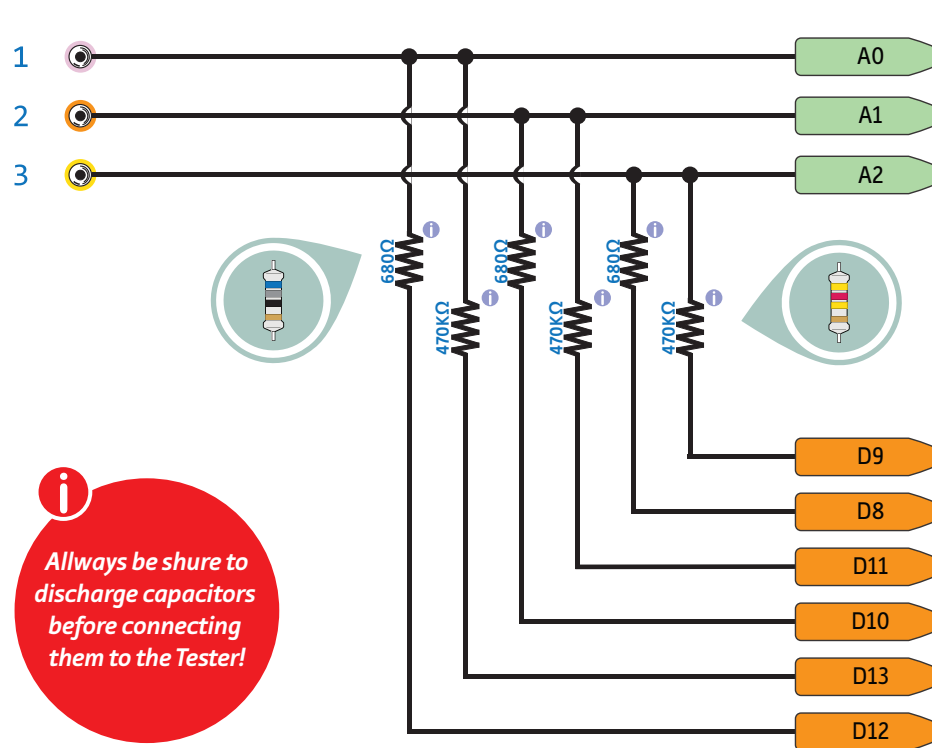

i
Allways be shure to
discharge capacitors
before connecting
them to the Tester!

i
To get full
accuracy
use 1% tolerance
resistors

i
Download sketch
at
at.pighixx.com