
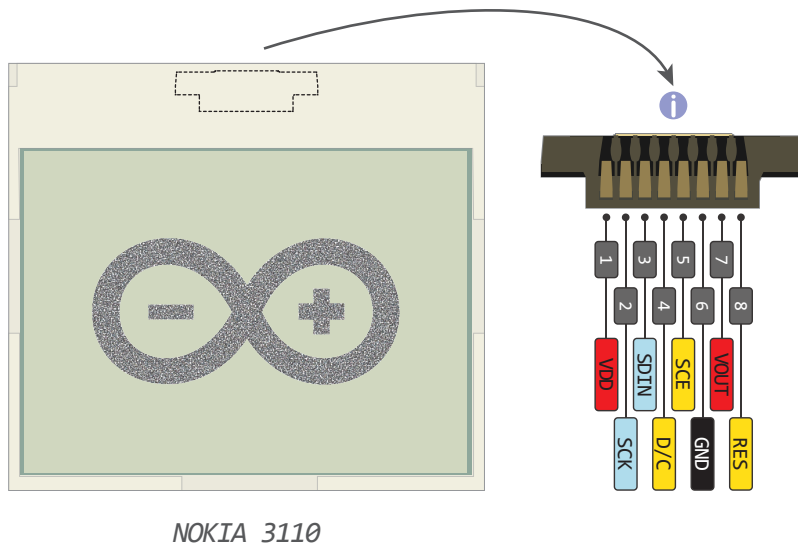


Connect a NOKIA LCD (Basic)



⚠ Only for 5V Arduino

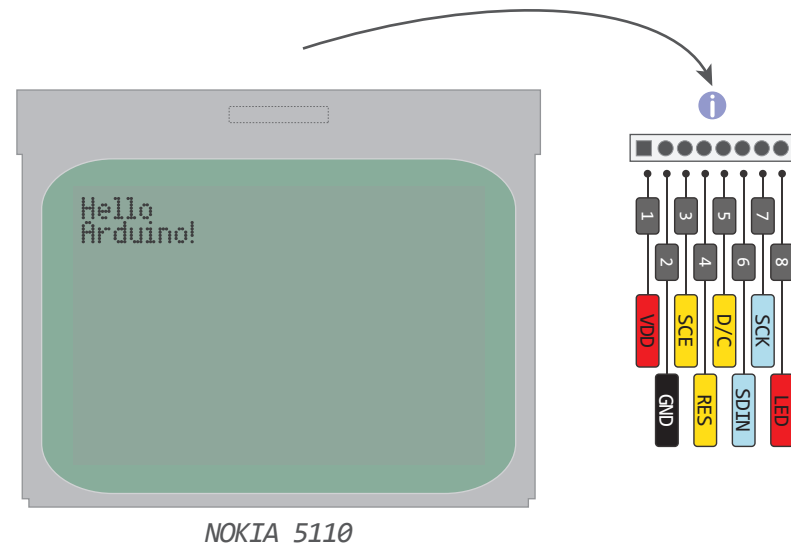



NOKIA 3110




NOKIA 5110

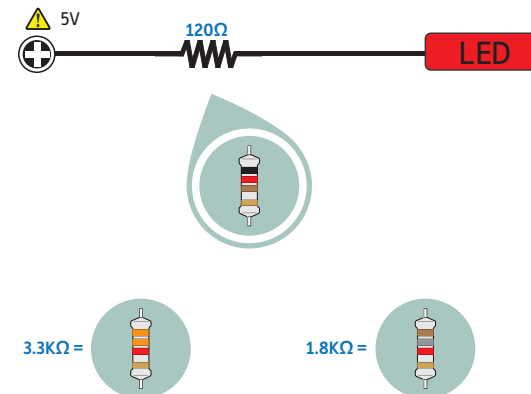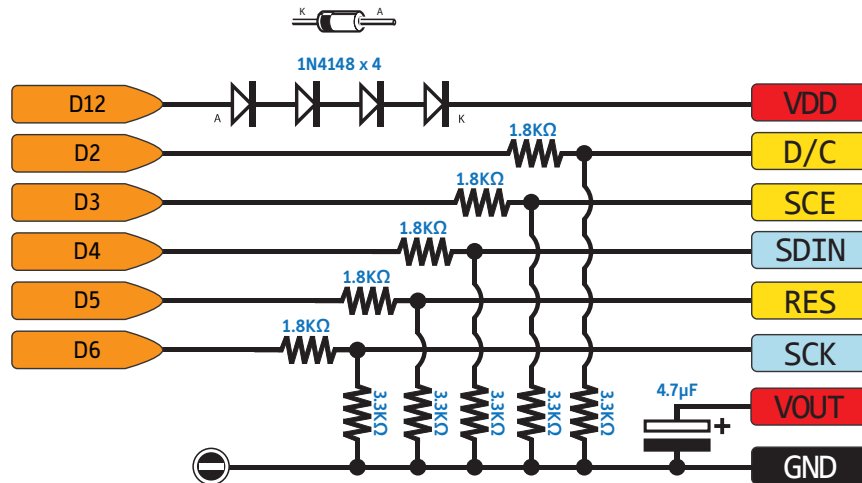

Drive a Unipolar Stepper (Basic 1)

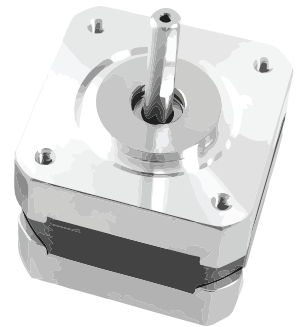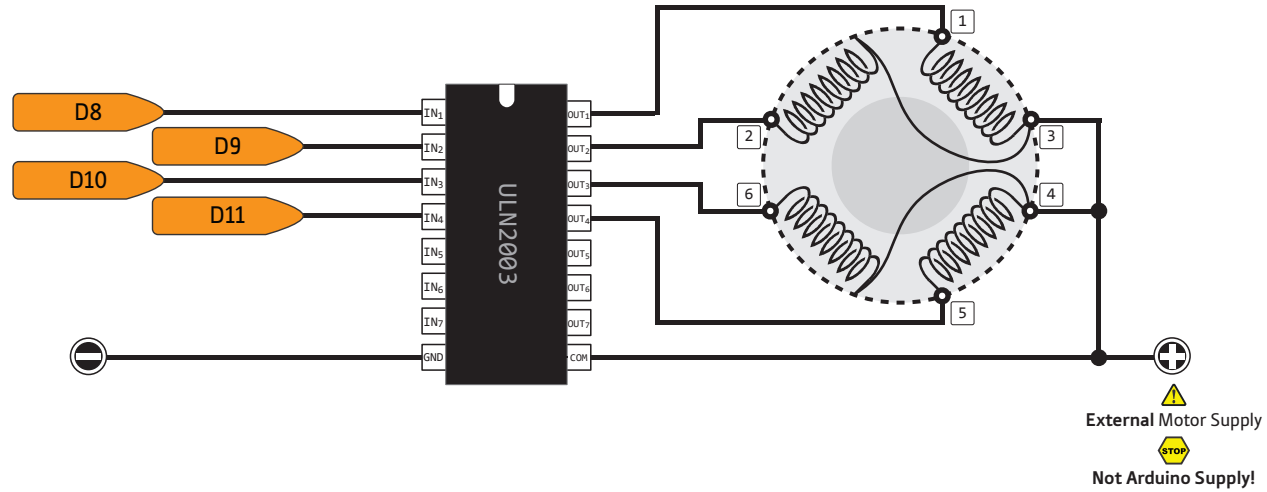

Drive a Bipolar Stepper (Basic 1)

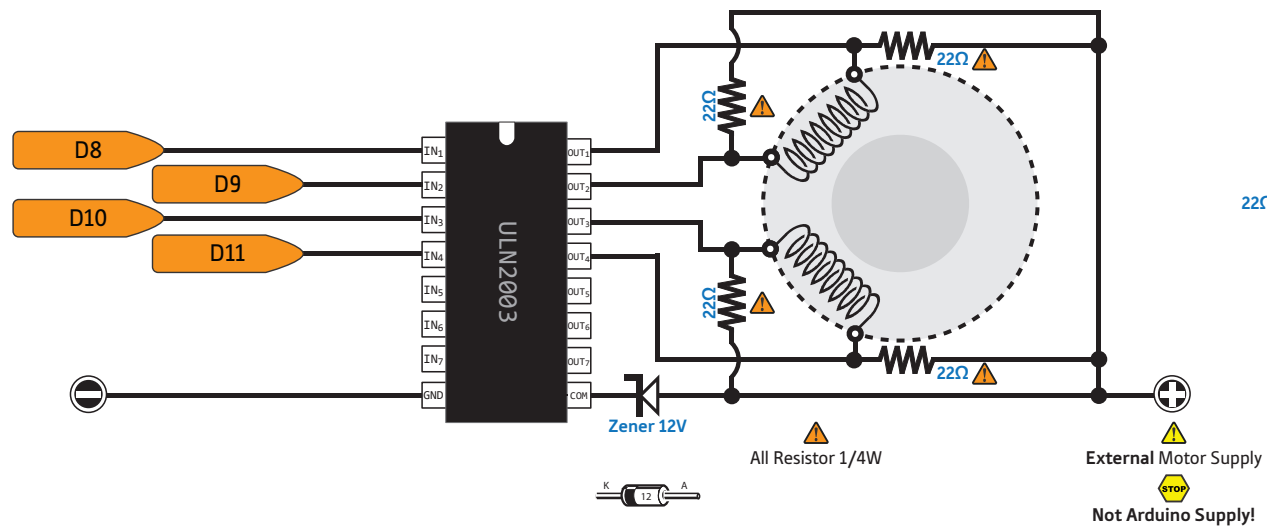

22Ω =



Connect a graphical LCD via I2C

